

## Serge Wave Multipliers

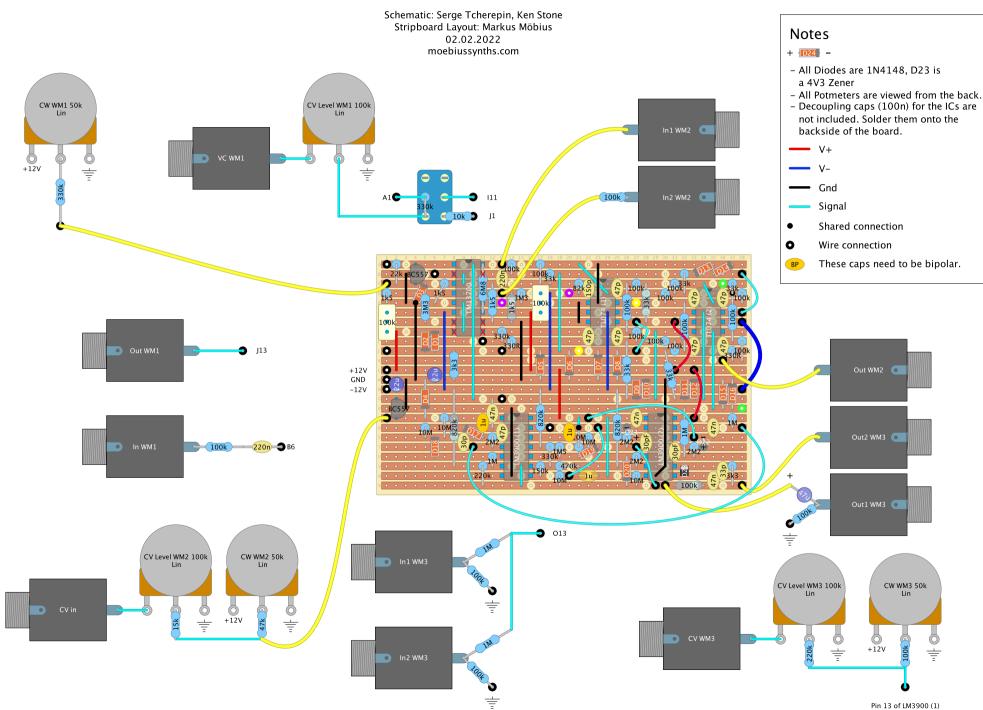

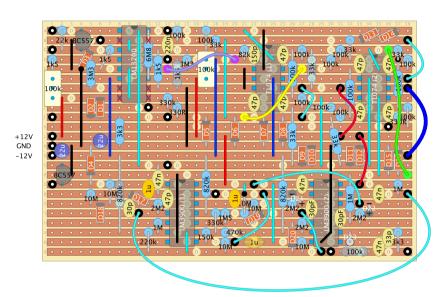
# Serge Wave Multipliers


Schematic: Serge Tcherepin, Ken Stone Stripboard Layout: Markus Möbius 02.02.2022 moebiussynths.com



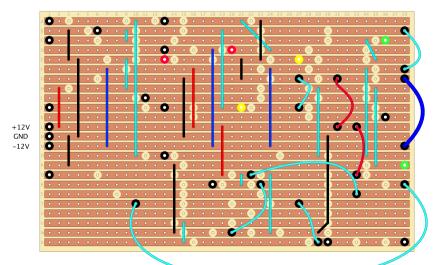
jumpers and line breakers only, viewed from the top



breakers only, viewed from the bottom

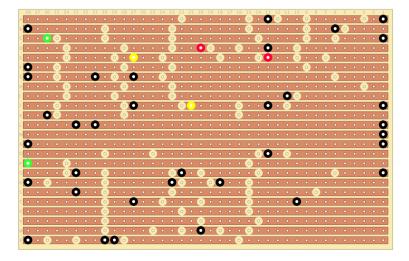


### **Top Wave Multiplier**

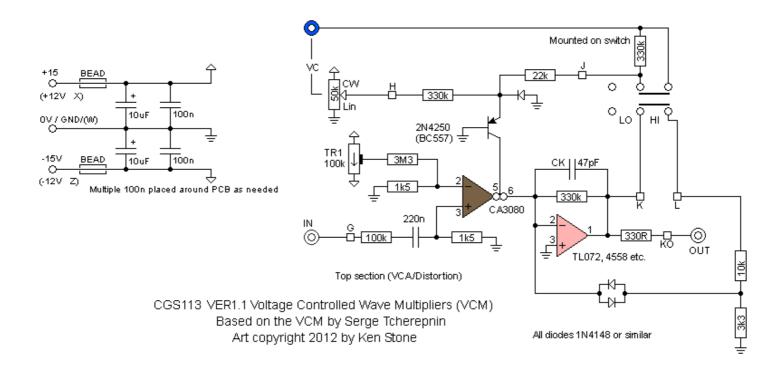

Source: https://www.elby-designs.com/webtek/cgs/serge/cgs113/cgs113 vcm.html


#### Middle Wave Multiplier

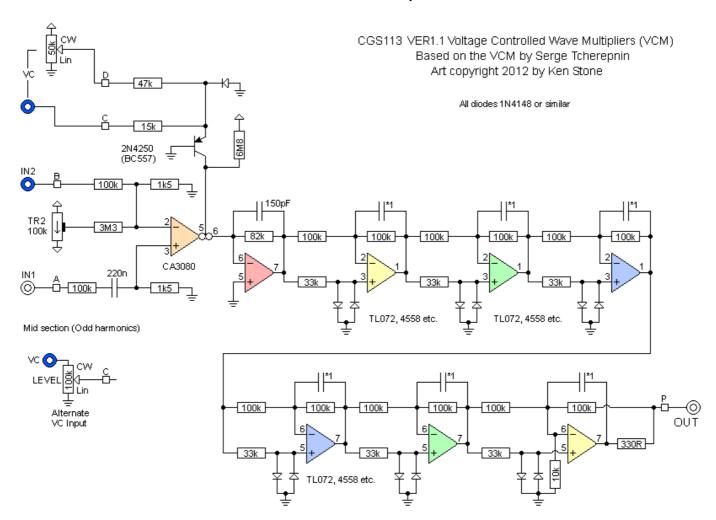

Caps marked with \*1 are 47p

Source: https://www.elby-designs.com/webtek/cgs/serge/cgs113/cgs113 vcm.html

#### **Bottom Wave Multiplier**

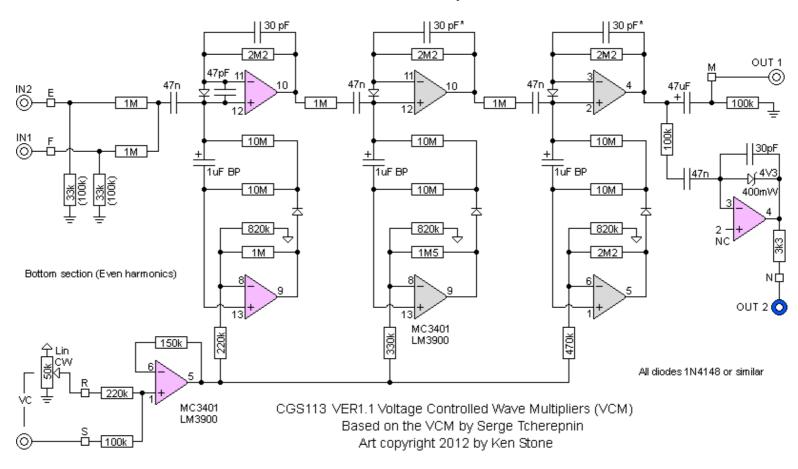

Source: https://www.elby-designs.com/webtek/cgs/serge/cgs113/cgs113\_vcm.html